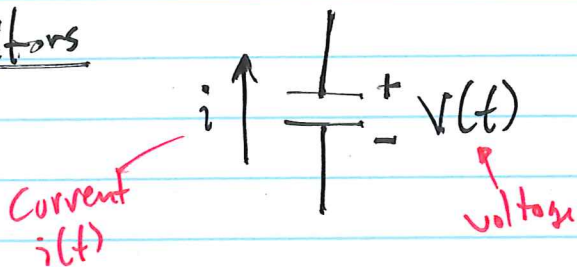


Math 152 - Lecture 24

Return to resistor networks, introduce time dependence

Capacitors




characterized by $V(t)$ which changes in time ~~is~~ in response to the current $i(t)$:

$$\frac{dV}{dt} = -\frac{i}{C}$$

constant, "capacitance" (Farads)

Inductor

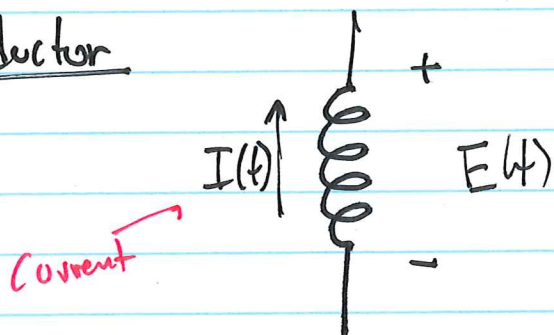

characterized by $I(t)$ changes according to the voltage $E(t)$

$$\frac{dI}{dt} = -\frac{E}{L}$$

constant "inductance" (Henry's)

At a moment in time t , inductor behaves like a current source $I(t)$ and a capacitor behaves like a voltage source. $V(t)$


Suppose we have some inductors, capacitors and resistors in network, (i 's)

Fundamental resistor network problem.

(A) determine the currents \wedge through the capacitors and the ~~voltages~~ voltages E 's across the inductors in terms of the V 's and I 's

(B) solve the DEs (with ICs)

Ex

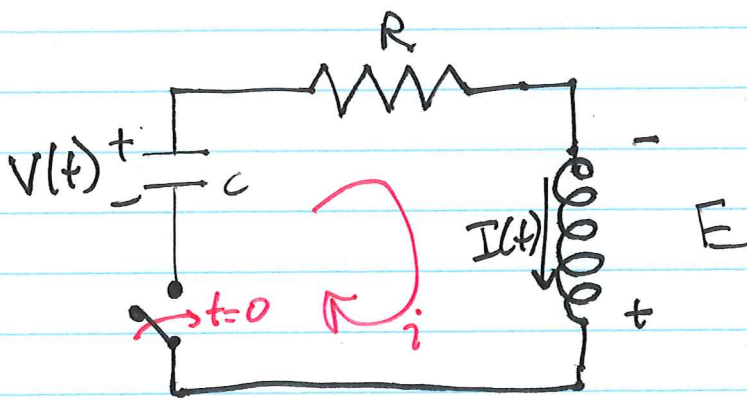

Initially, $V(0) = 1$
 $I(0) = 0$
 IC

(A) Fundamental Net. Prob. $iR - E - V(t) = 0$

and

$$i = I$$

$$\Rightarrow \boxed{E = IR - V}$$

(B)

$$\frac{dV}{dt} = -\frac{i}{C} = -\frac{I}{C}$$

$$\frac{dI}{dt} = -\frac{E}{L} = -\frac{(IR - V)}{L} = \frac{V}{L} - \frac{IR}{L}$$

DE

Rewrite as $\frac{d}{dt} \begin{bmatrix} I \\ V \end{bmatrix} = \underbrace{\begin{bmatrix} -R/L & 1/L \\ -1/C & 0 \end{bmatrix}}_A \begin{bmatrix} I \\ V \end{bmatrix}, \begin{bmatrix} I \\ V \end{bmatrix}(0) = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$

Eigenanalysis: $\det(A - \lambda I) = 0$

$$(-R/L - \lambda)(-\lambda) + 1/CL = 0 \Rightarrow \lambda^2 + \frac{R}{L}\lambda + \frac{1}{CL} = 0$$

$$\lambda_{1,2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{CL}}$$

(at least) two cases:

a) $\frac{1}{CL} < \frac{R^2}{4L^2} \Rightarrow \frac{R^2 C}{4L} > 1$ "large" resistance case

In this case, we have two ~~real~~ real, negative, and distinct eigenvalues strictly neg

$$\lambda_1 = -X + \sqrt{X^2 - \epsilon}, \quad \lambda_2 = -X - \sqrt{X^2 - \epsilon}$$

$$= -X + (X - \delta)$$

$$= -\delta$$

Sol'n: $\begin{bmatrix} I \\ V \end{bmatrix}(t) = c_1 \vec{v}_1 e^{\lambda_1 t} + c_2 \vec{v}_2 e^{\lambda_2 t}$ ★

φ
General Sol'n.

exponential decay. (as one might expect)

$$b) \quad \frac{R^2 C}{4L} < 1$$

$$\lambda_{1,2} = \frac{-R}{2L} \pm ib$$

$$b = \sqrt{\frac{1}{CL} - \frac{R^2}{4L^2}}$$

$$b \in \mathbb{R}$$

↑
exponential
decay, characteristic
time $\frac{2L}{R}$

↑
sin/cos
oscillation
with ~~period~~
period $2\pi/b$

For given R, C, L values, we would work out v_1 and v_2 , determine c_1 and c_2 to match the IC.

c) $\frac{R^2 C}{4L} = 1$ we have one \wedge ^{repeated} eigenvalue:

$$\lambda = -\frac{R}{2L} \pm 0$$

But it turns out there is no basis of eigenvectors \rightarrow matrix is defective and of no further concern for Math 152

(Pause for course evaluations — please do one :))

Ex above $R=2, L=2, C=1$

$$\lambda_{1,2} = -\frac{1}{2} \pm i\frac{1}{2} \quad \vec{v}_{1,2} = \begin{bmatrix} \frac{1}{2} \mp \frac{1}{2}i \\ 1 \end{bmatrix}$$

Recall we have an alternative form of the general sol'n.

$$\begin{aligned} \vec{v}_1 e^{\lambda_1 t} &= \vec{q}_1(t) + i \vec{q}_2(t) \\ &= e^{-t/2} \begin{bmatrix} \frac{1}{2} - \frac{1}{2}i \\ 1 \end{bmatrix} (\cos t/2 + i \sin t/2) \end{aligned}$$

$$= e^{-t/2} \begin{bmatrix} \frac{1}{2} \cos t/2 + \frac{1}{2} \sin t/2 \\ \cos t/2 \end{bmatrix} + i e^{-t/2} \begin{bmatrix} -\frac{1}{2} \cos t/2 + \frac{1}{2} \sin t/2 \\ \sin t/2 \end{bmatrix}$$

$\vec{q}_1(t)$
 $\vec{q}_2(t)$

General real sol'n is:

$$\begin{bmatrix} I \\ V \end{bmatrix}(t) = d_1 \vec{q}_1(t) + d_2 \vec{q}_2(t) \quad \star \star$$

$\downarrow \mathbb{R}$ $\downarrow \mathbb{R}^2$ $\downarrow \mathbb{R}$ $\downarrow \mathbb{R}^2$

Sol'n: Use IC $= \begin{bmatrix} 0 \\ 1 \end{bmatrix} = d_1 \vec{q}_1(0) + d_2 \vec{q}_2(0)$


$$\begin{bmatrix} 0 \\ 1 \end{bmatrix} = d_1 \begin{bmatrix} \frac{1}{2} \\ 1 \end{bmatrix} + d_2 \begin{bmatrix} -\frac{1}{2} \\ 0 \end{bmatrix}$$

by inspection: $d_1=1$ and $d_2=1$


$$\begin{bmatrix} I \\ V \end{bmatrix}(t) = e^{-t/2} \begin{bmatrix} \cancel{\frac{1}{2} \cos t/2} + \frac{1}{2} \sin t/2 - \cancel{\frac{1}{2} \cos t/2} + \frac{1}{2} \sin t/2 \\ \cos t/2 + \sin t/2 \end{bmatrix}$$

plot, etc

Ex $C=1$, $L=10$

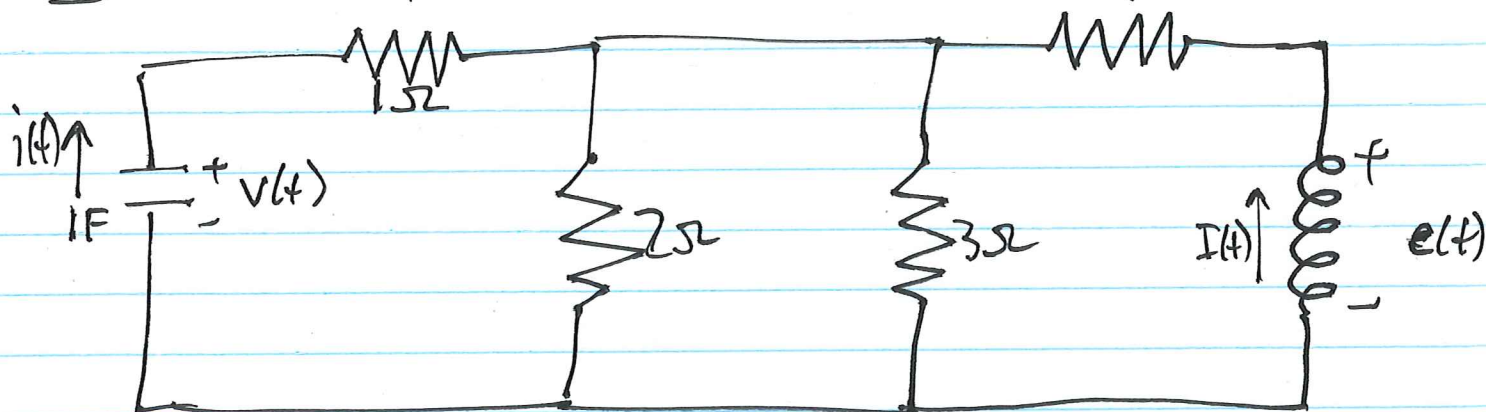

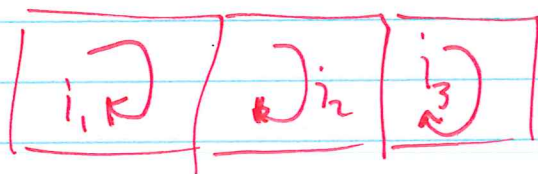We did ~~this~~ the static case before in lecture 09



$$\begin{aligned} 1i_1 + 2(i_2 - i_3) - V &= 0 \\ 2(i_2 - i_1) + 3(i_2 - i_3) &= 0 \\ 5i_3 + e + 3(i_3 - i_2) &= 0 \end{aligned}$$

$i_3 = -I$
 called "v_i"
 in lecture 9

... GE ...

(Fundamental Net Prob)

$$\begin{cases} i = i_1 = \frac{5}{36} V - \frac{1}{6} I \\ e = \frac{1}{6} V + 6 I \end{cases}$$

These go into the RHS of the DEs:

$$\frac{dV}{dt} = \frac{-i}{C} = -\frac{5}{36} V + \frac{1}{6} I$$

$$\frac{dI}{dt} = \frac{-e}{L} = -\frac{1}{60} V + \frac{6}{10} I$$

time scales

Eigenvalues: $\lambda_1 \approx -0.5939$, $\lambda_2 \approx -0.1450$
 \Rightarrow decay, no oscillations, ~~transient~~ decay happens on $\frac{1}{|\lambda_1|} \approx 7s$