

Outline

Week 5: Circuits

Course Notes: 3.5

Goals: Use linear algebra to determine voltage drops and branch currents.


Components in Resistor Networks





Components in Resistor Networks




Components in Resistor Networks

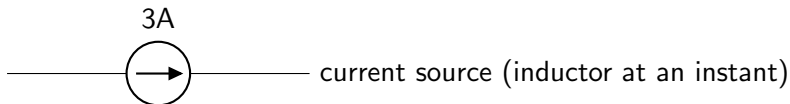


Components in Resistor Networks

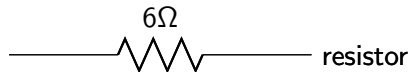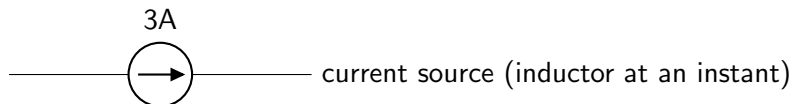


$$V = IR$$

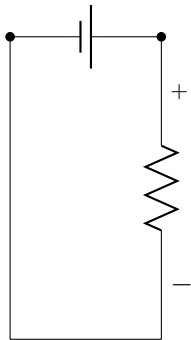


$$V = IR$$

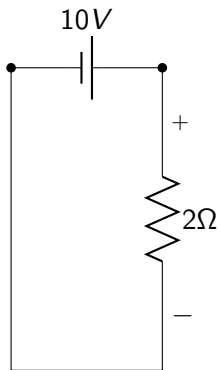


$$V = IR$$

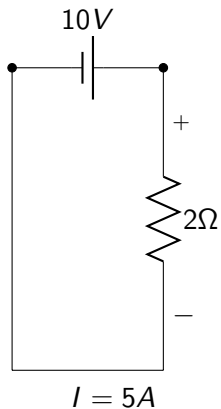


$$V = IR$$

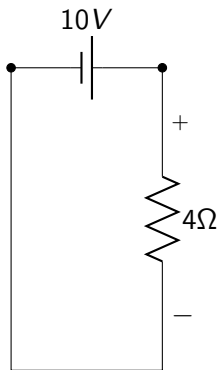


$$V = IR$$

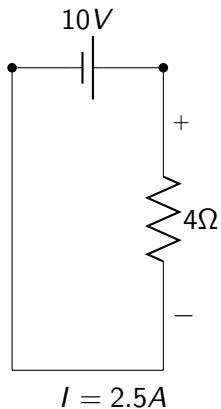


$$V = IR$$

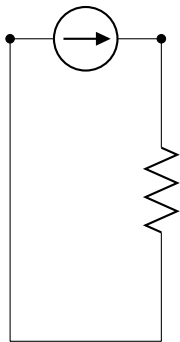

$$V = IR$$

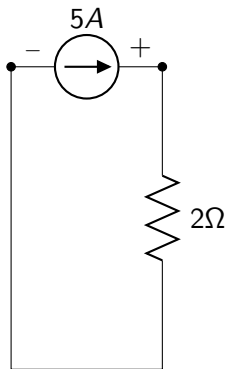


$$V = IR$$

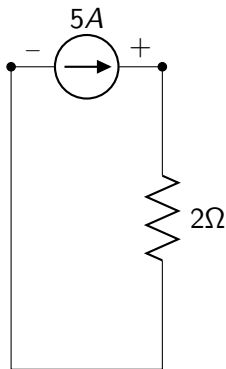

$$V = 10$$

(voltage drop of 10 Volts across resistor)


$$V = IR$$

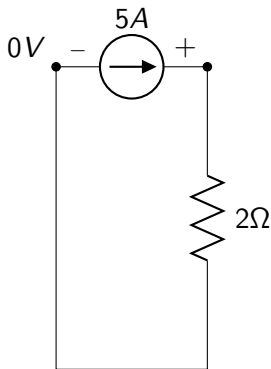

$$V = 10$$


(voltage drop of 10 Volts across resistor)

$$V = IR$$

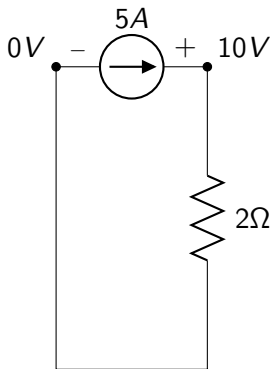

$V = 10$
(voltage drop of 10 Volts across resistor)

$$V = IR$$

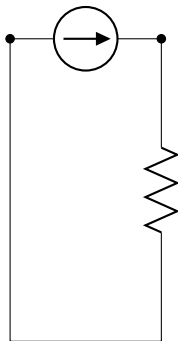



Setup: Given: Resistance of resistors; voltage across voltage sources; current through current sources.


Find: currents through each resistor and each power source; voltage drops across each current source


Kirchhoff's Laws

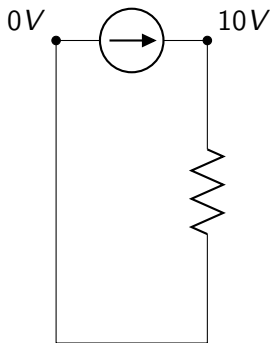1. The sum of voltage drops around any closed loops in the network must be zero.
2. For any node, current in equals current out




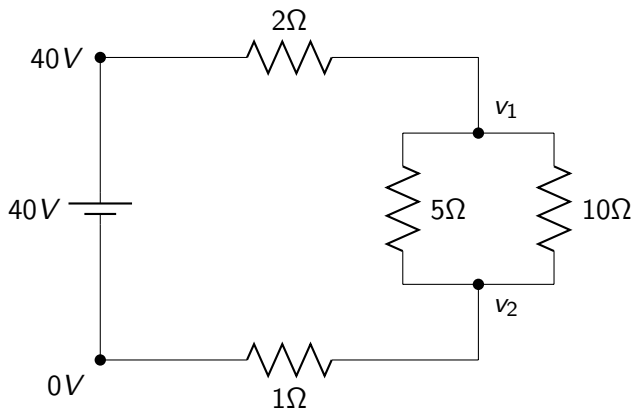

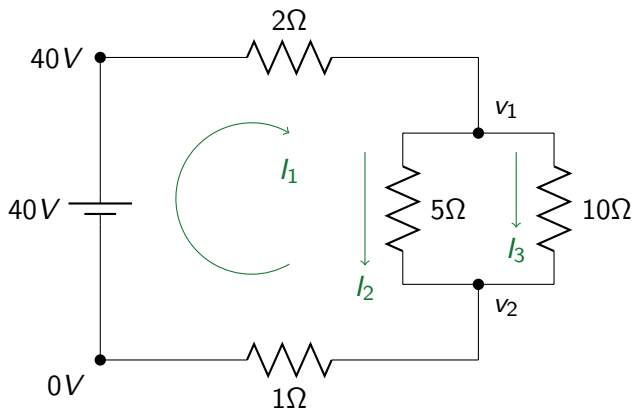

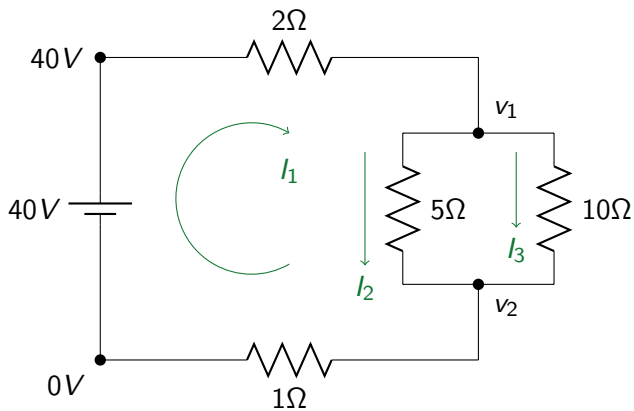
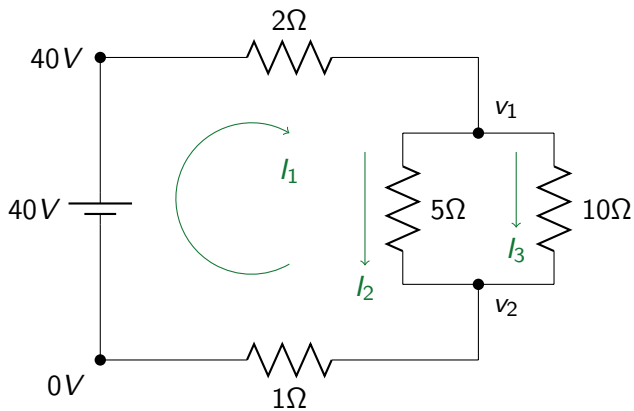
$$\begin{aligned} i_1 &= i_2 + i_3 \\ 40 - v_1 &= i_2 \cdot 2 \\ v_2 - 0 &= i_1 \cdot 1 \\ v_1 - v_2 &= 5i_2 \\ v_1 - v_2 &= 10i_3 \end{aligned}$$



$$i_1 = i_2 + i_3$$

$$40 - v_1 = i_2 \cdot 2$$

$$v_2 - 0 = i_1 \cdot 1$$

$$v_1 - v_2 = 5i_2$$

$$v_1 - v_2 = 10i_3$$


$$i_1 \approx 6.3$$

$$i_2 \approx 4.2$$

$$i_3 \approx 2.1$$

$$v_1 \approx 27.4$$

$$v_2 \approx 6.3$$

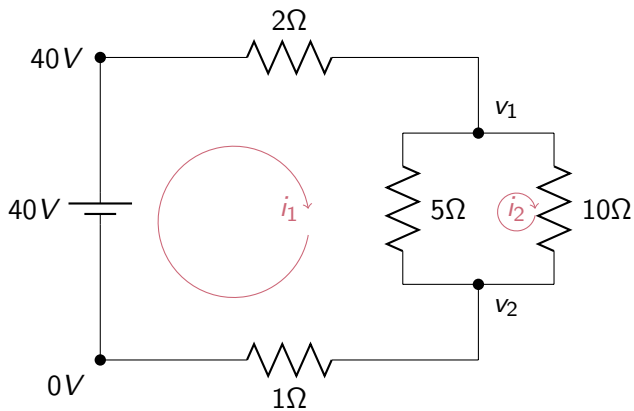

$$i_1 = i_2 + i_3$$

$$40 - v_1 = i_2 \cdot 2$$

$$v_2 - 0 = i_1 \cdot 1$$

$$v_1 - v_2 = 5i_2$$

$$v_1 - v_2 = 10i_3$$


$$i_1 \approx 6.3$$

$$i_2 \approx 4.2$$

$$i_3 \approx 2.1$$

$$v_1 \approx 27.4$$


$$v_2 \approx 6.3$$

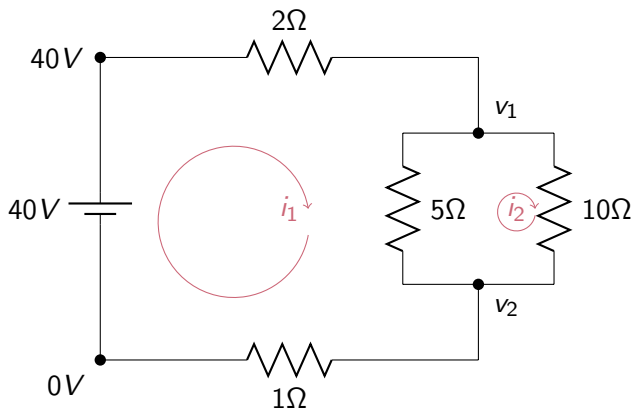



$$\begin{aligned}
 i_1 &= i_2 + i_3 \\
 40 - v_1 &= i_2 \cdot 2 \\
 v_2 - 0 &= i_1 \cdot 1 \\
 v_1 - v_2 &= 5i_2 \\
 v_1 - v_2 &= 10i_3
 \end{aligned}$$

$$\begin{aligned}
 i_1 &\approx 6.3 \\
 i_2 &\approx 4.2 \\
 i_3 &\approx 2.1 \\
 v_1 &\approx 27.4 \\
 v_2 &\approx 6.3
 \end{aligned}$$

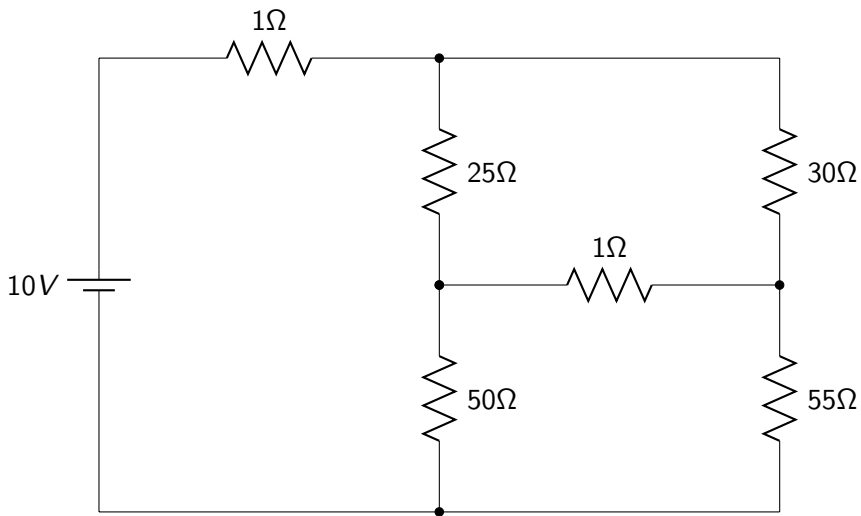
$$\begin{aligned}
 1i_1 - 40 + 2i_1 + 5(i_1 - i_2) &= 0 \\
 10i_2 + 5(i_2 - i_1) &= 0
 \end{aligned}$$




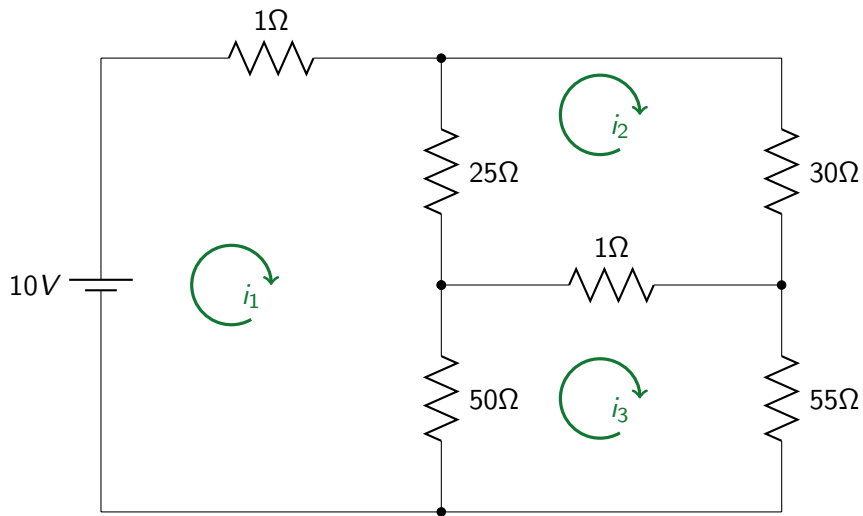


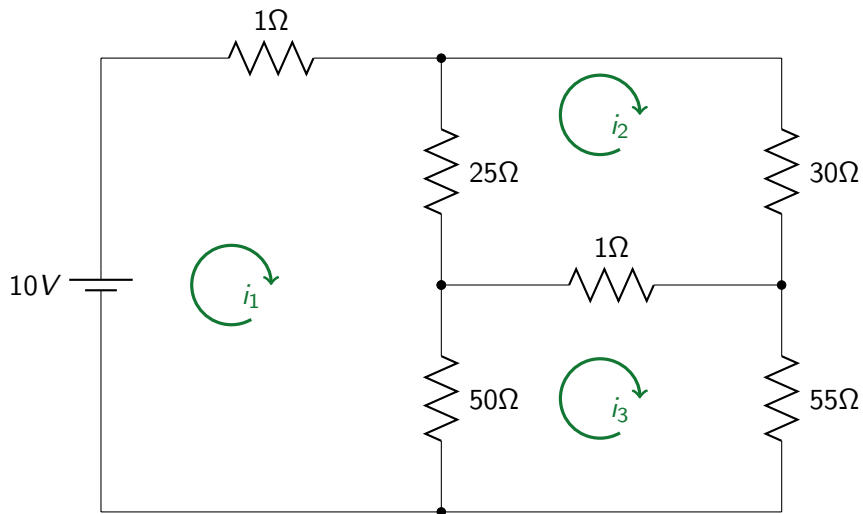

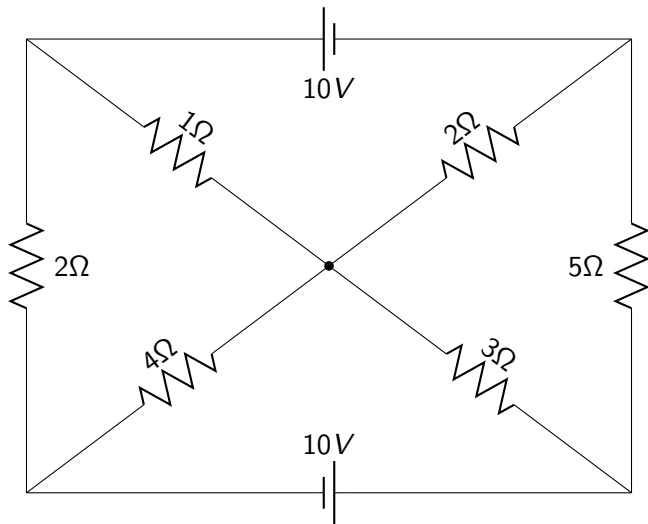
$$i_1 \approx 0.2249, \quad i_2 \approx 0.1114, \quad i_3 \approx 0.1166$$




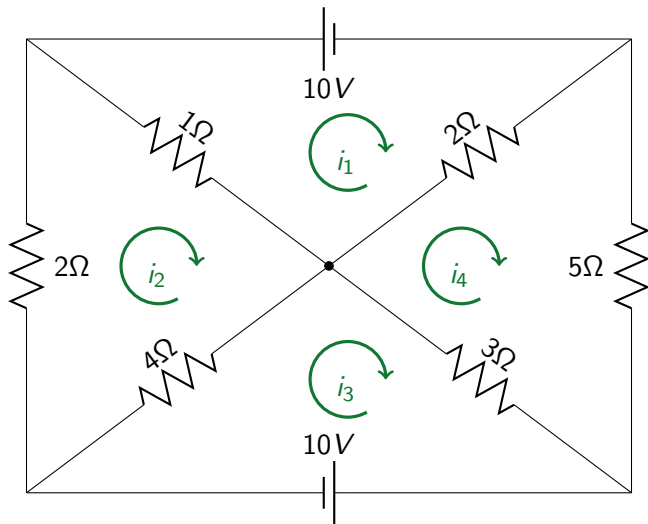


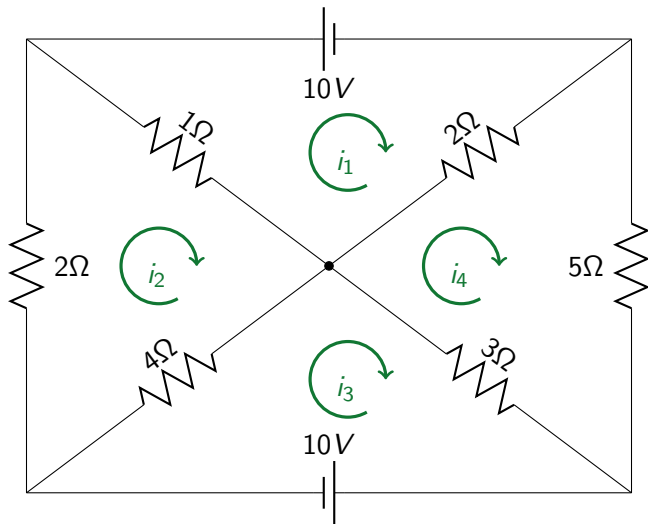

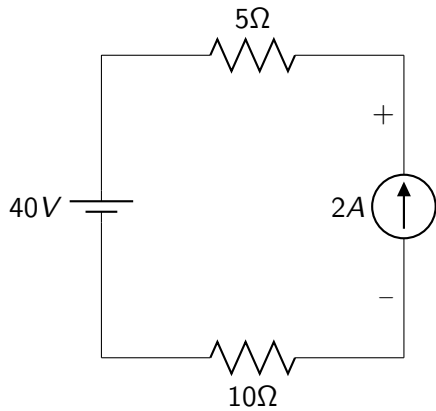
$$i_1 = -3.3036 \quad i_2 = 0.4464 \quad i_3 = 1.6071 \quad i_4 = -0.1786$$




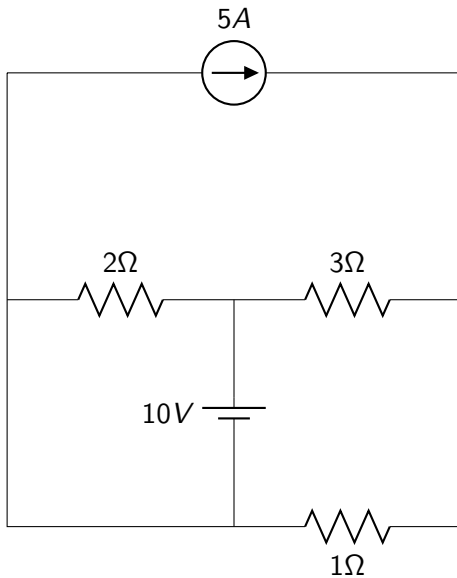


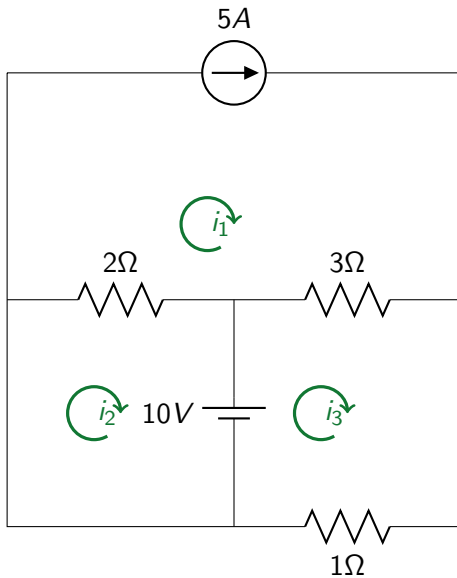


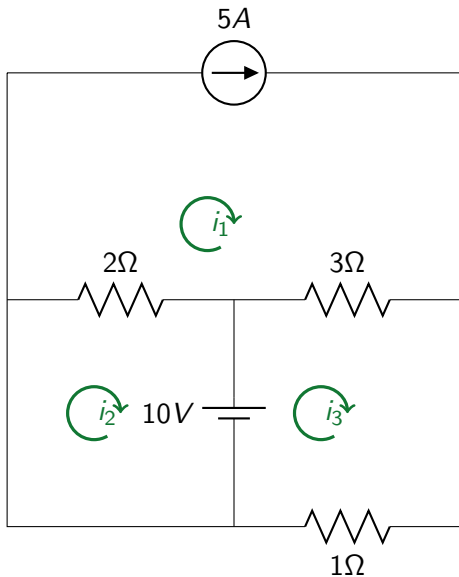

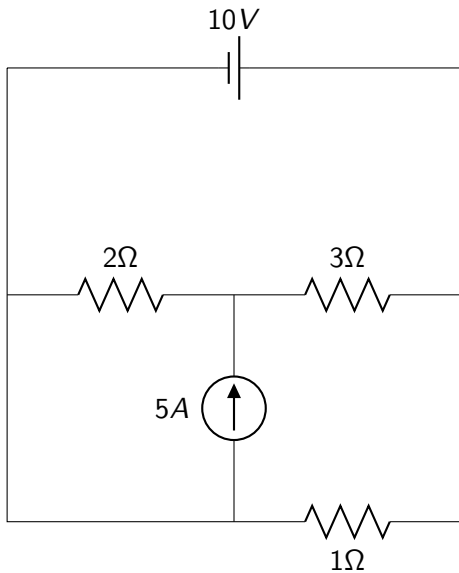
$$i_1 = 5, \quad i_2 = 0, \quad i_3 = \frac{25}{4}$$



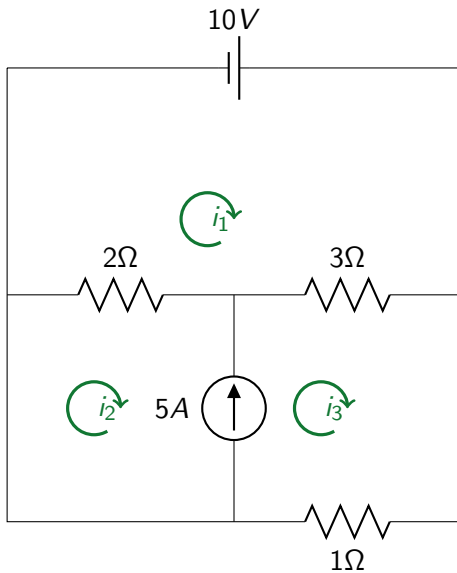

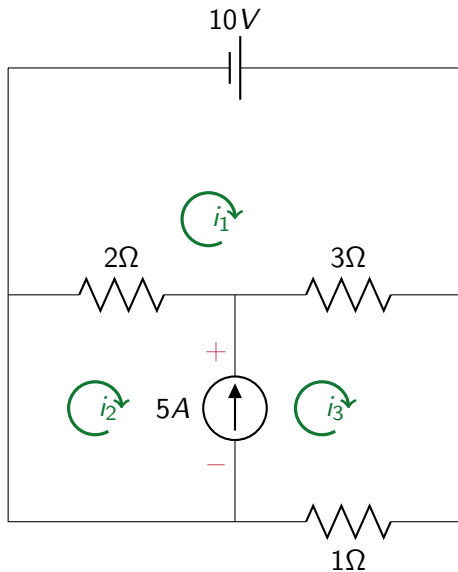


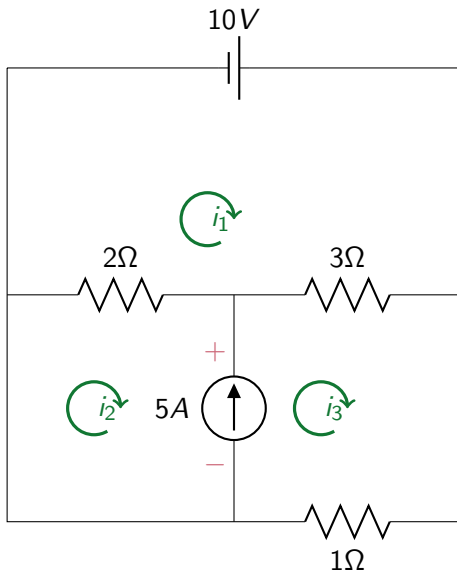
Let E be the voltage drop across the current source.




Let E be the voltage drop across the current source.

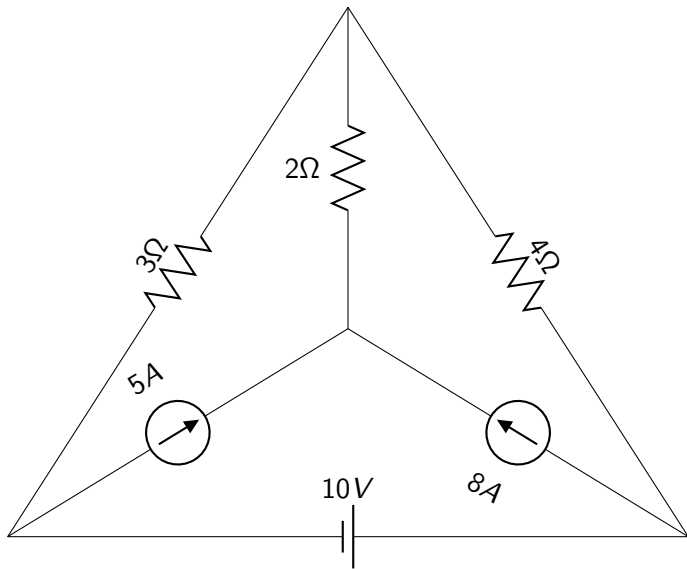
$$i_1 = 10, \quad i_2 = 5, \quad i_3 = 10, \quad E = 10$$




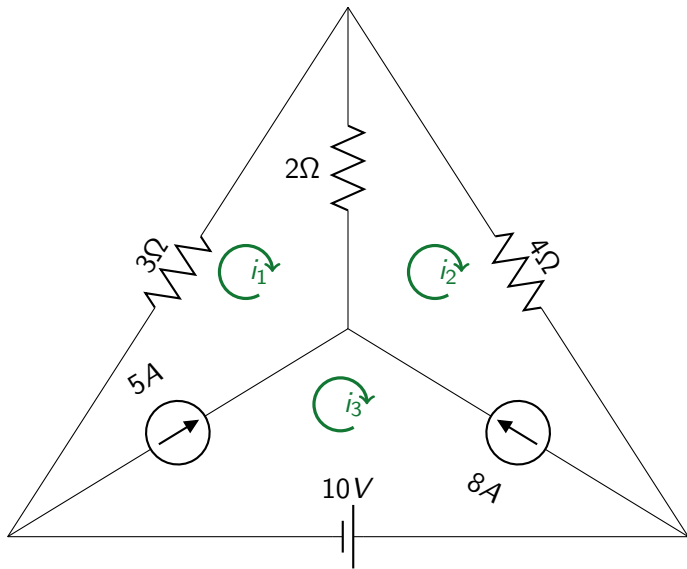


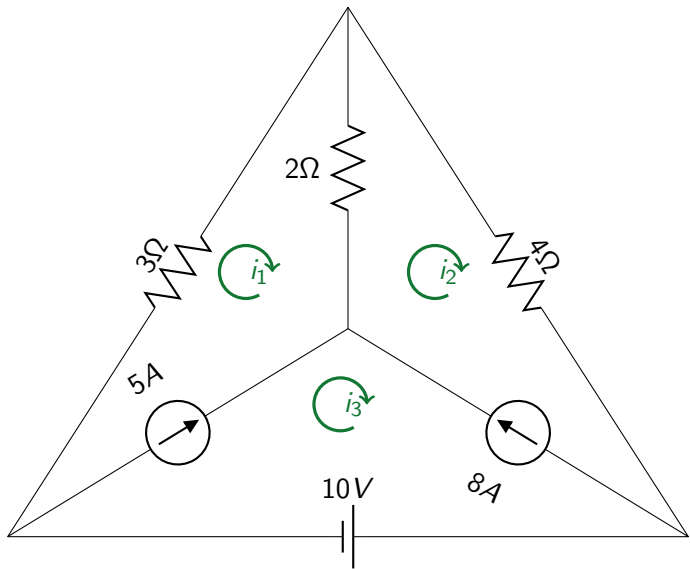
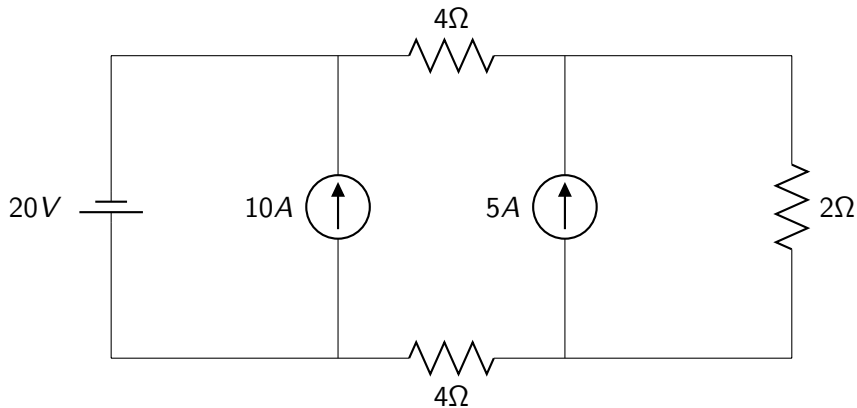
$$i_1 = -8.8571, \quad i_2 = 4.1429, \quad i_3 = -3.8571, \quad E_1 = 52.5744, \quad E_2 = 42.5714$$




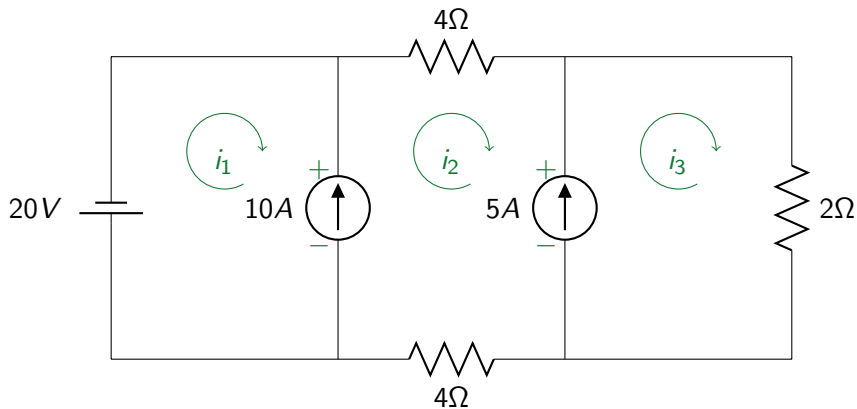


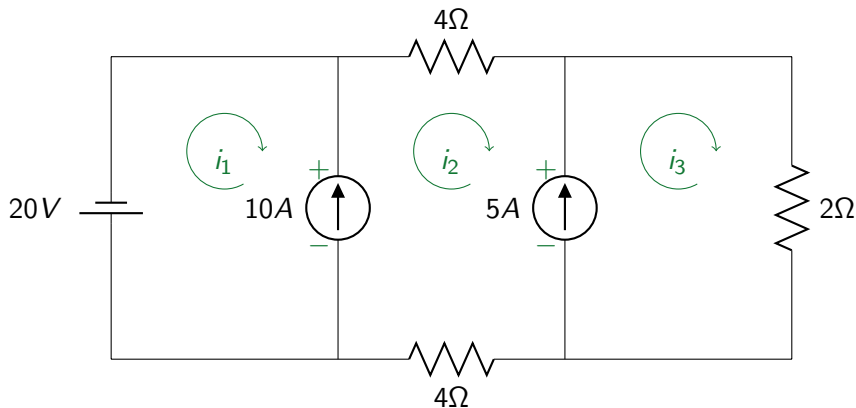


$$i_1 = -13A, \quad i_2 = -3A, \quad i_3 = 2A, \quad E_1 = -20V, \quad E_2 = 4V$$

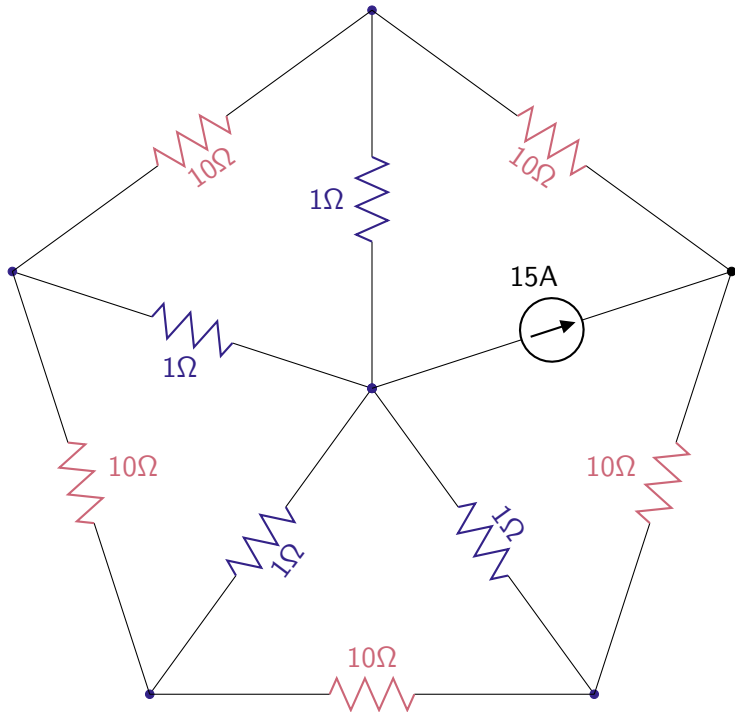Current across voltage source: 13A, top to bottom




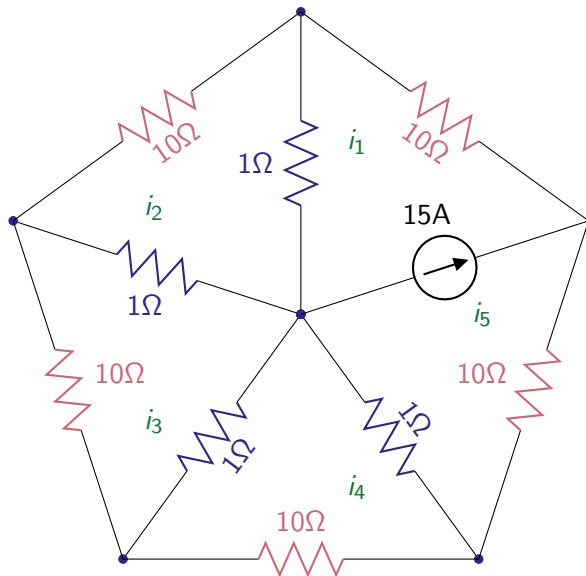

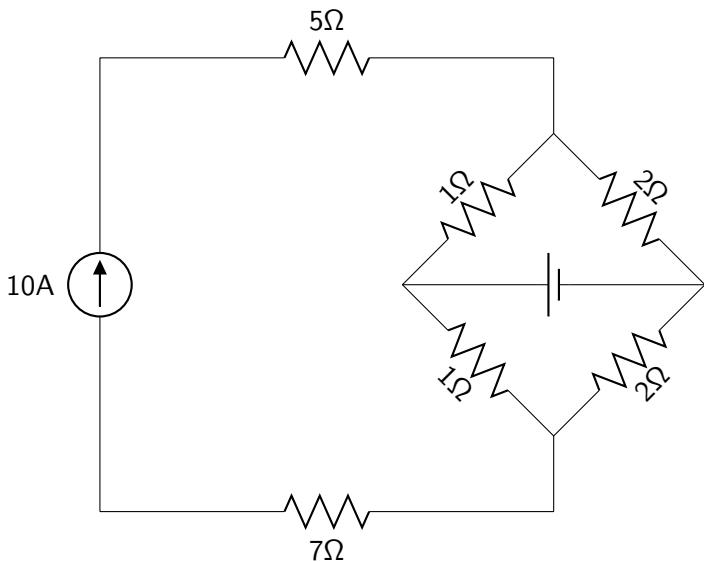
clockwise: $i_1 = -7.5$, $i_2 = -0.625$, $i_3 = 0$, $i_4 = 0.625$, $i_5 = 7.5$



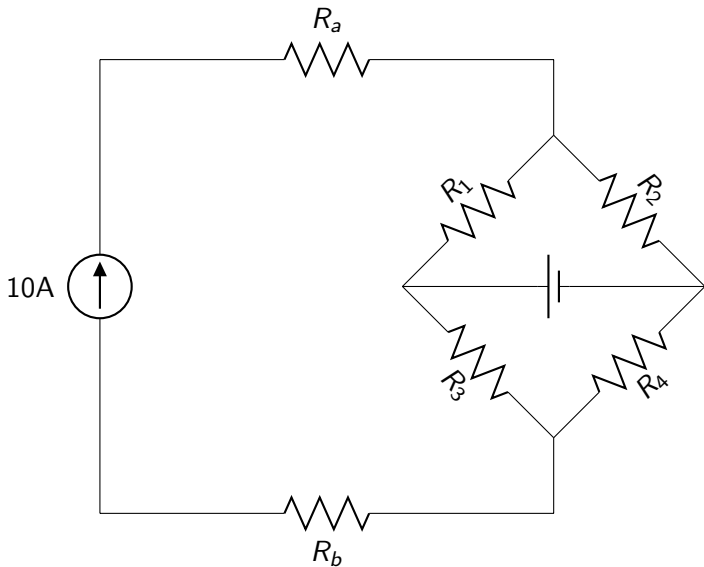
What voltage should the voltage source have, in order for there to be no current across it?



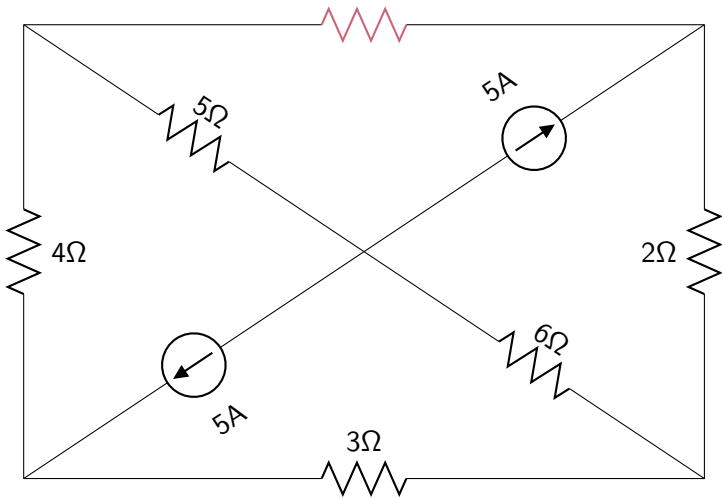What voltage should the voltage source have, in order for there to be no current across it?




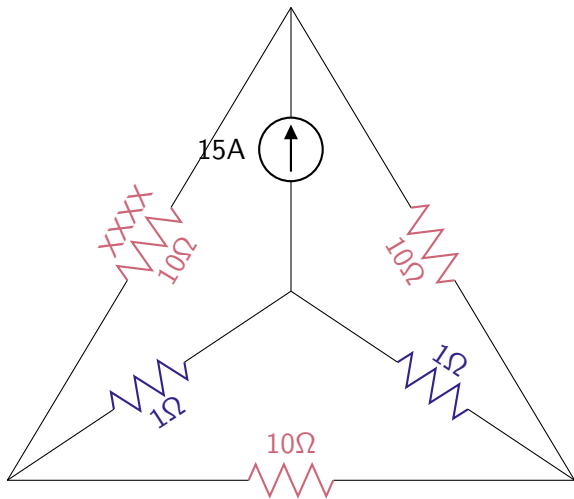What resistance should the top resistor have, if you want each wire touching the centre to have current 5A ?



Replace ONE resistor (with a different resistor or a different component) so that the current through the marked resistor is zero.

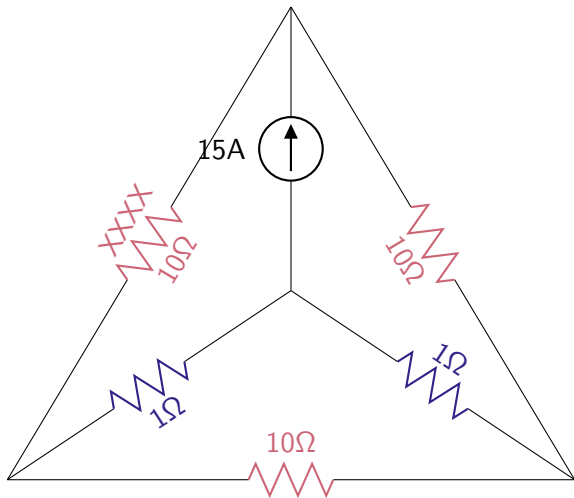(OK fine, one way is to remove the marked resistor itself. Try something else :))



Find all ways to change the resistances of the non-marked resistors so that the current flowing through the marked resistor is zero. Justify your answer with algebra.

